# **Current Limiter with Active Damping for Dimmable Lighting Systems**

#### Description

- Lighting systems, such as an LED driver, can utilize a current limiter for surge protection and active damping
- Current limiter includes a switchable resistor whose impedance can be varied by either a surge control or a damper control circuit
- Surge control circuit can increase the impedance of the switchable resistor when the rectified voltage V<sub>RECT</sub> is greater than a surge threshold
- Damper control circuit can increase the impedance of the switchable resistor after the dimmer circuit switches on to dampen input current I<sub>IN</sub>.
- Damper control circuit can reduce the impedance when V<sub>RECT</sub> reaches a damper threshold to stop damping

### Benefits

- Allows a lighting system to withstand high energy surges while simultaneously providing active damping for dimmer circuits
- Improves overall efficiency
- Could be used with: LED drivers, LinkSwitch-PH, LinkSwitch-PL



Figure 1. Lighting system with a current limiter which includes a switchable resistor, surge control, and damper control

US 9,332,613 Rev: 1; MAY 2019; PI.0373 World Headquarters 5245 Hellyer Avenue, San Jose, CA 95138, USA, Main: +1-408-414-9200

1 Customer Service Phone: +1-408-414-9665, Fax: +1-408-414-9765, Email: <u>info@power.com</u> On the Web <u>www.power.com</u>

## **Example Current Limiter with Active Damping**

### Low side coupled switchable resistor, includes R9, VR2 and Q3

Q3 varies impedance of the current limiter by turning ON or OFF; impedance equal to R9 when Q3 is OFF, R9 shorted when Q3 is ON

### Surge control circuit includes R3, R4, R5, VR1 and Q2

- Adjusts voltage at the control input of Q3 in response to voltage across R5
- Q3 is turned off when the voltage across R5 is greater than or equal to the sum of the breakdown voltage of VR1 and the turn on voltage of Q2

### Damper control circuit includes R6, R7, R8, D1, Q1 and C1

- ▶ When dimmer circuit is first turned ON, Q3 is turned OFF
- Q3 turns ON when the voltage across C1 reaches a damper threshold
- Q1 is turned ON to discharge C1 when voltage on C1 exceeds the voltage across R8 by the turn-on voltage of Q1





US 9,332,613 Rev: 1; MAY 2019; PI.0373

2